

Chapter 31 Inductance

31.1 Self-Induction and Inductance

Self-Inductance

$$\Phi_m = BA = \mu_0 nIA \propto I \quad \rightarrow \quad \Phi_m = LI$$

The unit of the inductance is henry (H). $1\text{H} = 1 \frac{\text{Wb}}{\text{A}} = 1 \frac{\text{T} \cdot \text{m}^2}{\text{A}}$

When the current in the circuit is changing, the magnetic flux is also changing.

$$\frac{d\Phi}{dt} = \frac{d(LI)}{dt} = L \frac{dI}{dt} \quad \rightarrow \quad \text{The induced emf should be } \varepsilon = -\frac{d\Phi}{dt} = -L \frac{dI}{dt}$$

The self inductance of a infinite long solenoid:

$$\Phi_m = NAB = NA\mu_0 \frac{N}{l} I = \mu_0 A \frac{N^2}{l} I \quad \rightarrow \quad L = \frac{\Phi_m}{I} = \mu_0 A \frac{N^2}{l}$$

$$\varepsilon = -L \frac{dI}{dt}$$


Considering the inductor having an internal resistance r , the potential difference is:

$$\Delta V = \varepsilon - Ir = -L \frac{dI}{dt} - Ir$$

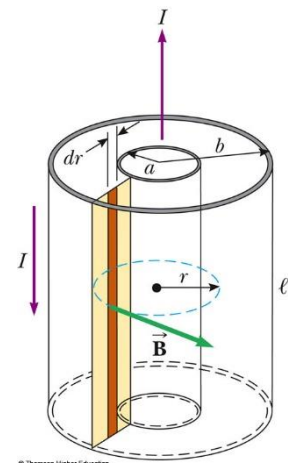Example: Model a long coaxial cable as two thin, concentric, cylindrical conducting shells of radii a and b and length l . The conducting shells carry the same current in opposite directions. Calculate the inductance L of this cable.

Calculate magnetic flux:

$$B = \frac{\mu_0 I}{2\pi r} \quad \rightarrow \quad \Phi = \int_0^l \int_a^b \frac{\mu_0 I}{2\pi r} dr dz = \frac{\mu_0 I}{2\pi} l \ln\left(\frac{b}{a}\right)$$



$$\Phi = LI \rightarrow L = \frac{\mu_0 l}{2\pi} \ln\left(\frac{b}{a}\right)$$

31.2 RL Circuits

Use Kirchhoff's rule:

$$\oint \vec{E} \cdot d\vec{l} = 0$$


$$\varepsilon_0 - IR - L \frac{dI}{dt} = 0$$

$$\text{Differential Eq: } \varepsilon_0 - IR - L \frac{dI}{dt} = 0 \rightarrow \varepsilon_0 - IR = L \frac{dI}{dt}$$

$$\rightarrow dt = L \frac{dI}{(\varepsilon_0 - IR)} \rightarrow dt = -\frac{L}{R} \frac{d(\varepsilon_0 - IR)}{(\varepsilon_0 - IR)}$$

$$\rightarrow -\frac{R}{L} t = \ln\left(\frac{\varepsilon_0 - IR}{\varepsilon_0}\right) \rightarrow \varepsilon_0 - IR = \varepsilon_0 e^{-\frac{R}{L}t} \rightarrow I = \frac{\varepsilon_0}{R} \left(1 - e^{-\frac{R}{L}t}\right)$$
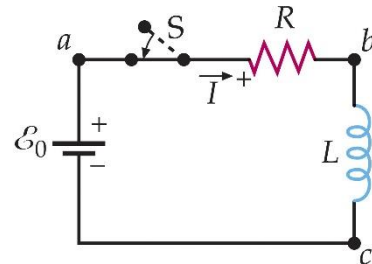
$$\text{Time constant: } \tau = \frac{L}{R}$$



Example: Find the total energy dissipated in the resistor R, when the current in the inductor decreases from its initial value of I_0 to 0?

$$I = \frac{\varepsilon_0}{R} e^{-\frac{R}{L}t}, \quad P = I^2 R \rightarrow U = \int_0^{\infty} I_0^2 e^{-2\frac{R}{L}t} R dt = \frac{1}{2} LI_0^2$$

31.3 Energy in a Magnetic Field

Obtain the magnetic energy from the emf induced by self inductance.

$$\Phi_m = LI \rightarrow \text{The induced emf is } \varepsilon = -\frac{d\Phi_m}{dt} = -L \frac{dI}{dt}$$

$$\text{The energy dissipated or the power is } P = IV = I\varepsilon = -LI \frac{dI}{dt}$$

The total energy when the current has reached its final value I_f is:

$$U = \int_{t=0}^{t=f} \left(LI \frac{dI}{dt} \right) dt = \int_{I=0}^{I=f} LI dI = \frac{1}{2} LI^2$$

Calculate the magnetic energy by obtaining the energy stored in the self inductor of an infinite solenoid.

$$B = \mu_0 n I, \quad \Phi = n l A (\mu_0 n I) = L I$$

$$U = \frac{1}{2} L I^2 = \frac{1}{2} \mu_0 n^2 (A l) I^2 = u_m V$$

$$u_m = \frac{1}{2} \mu_0 n^2 I^2 = \frac{B^2}{2 \mu_0} \quad \langle \text{----} \rangle \quad u_e = \frac{1}{2} \epsilon_0 E^2 \quad (\text{Do you remember how to get this?})$$

Example: A certain region of space contains a uniform magnetic field of 0.020 T and a uniform electric field of 2.5×10^6 N/C. Find (a) the total electromagnetic density.

$$u_e = \frac{1}{2} \epsilon_0 E^2 = \frac{1}{2} (8.85 \times 10^{-12}) (2.5 \times 10^6)^2 = 27.7 \text{ J/m}^3$$

$$u_m = \frac{B^2}{2 \mu_0} = \frac{(0.02)^2}{2(4\pi \times 10^{-7})} = 159 \text{ J/m}^3$$

31.4 Mutual Inductance

Mutual Inductance

The magnetic field of loop 1 is: $B \sim \frac{\mu_0 I_1}{2R}$

The flux at 2 is $\Phi_2 \sim \frac{\mu_0 I_1}{2R} \pi R^2 = \mu_0 \frac{\pi R^2}{2} I_1 = I_1 M_{12}$



The flux at 1 is $\Phi_1 \sim \mu_0 \frac{\pi R^2}{2} I_2 = I_2 M_{21}$


The concept of inductance: $\Phi = M I$

$M_{12} = M_{21}$ --> The mutual inductance is determined when the geometrical configuration between the two loops is given.

B in 1 due to 2: $B = \mu_0 \frac{N_2}{l} I_2$

Flux in 1: $\Phi = N_1 (\pi r_1^2) \left(\mu_0 \frac{N_2}{l} I_2 \right) = I_2 M_{21}$

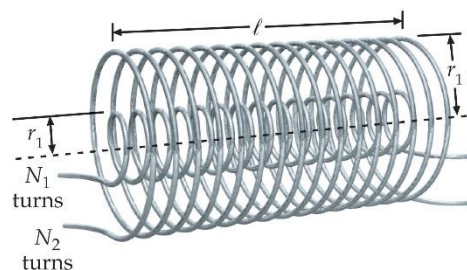B in 2 due to 1: $B = \mu_0 \frac{N_1}{l} I_1$



Flux in 2: $\Phi = N_2 \left(\pi r_1^2 \right) \left(\mu_0 \frac{N_1}{l} I_1 \right) = I_1 M_{12}$

$$M_{12} = M_{21} = \mu_0 \left(\pi r_1^2 \right) \frac{N_1 N_2}{l}$$

31.5 Oscillations in an LC Circuit

Kirchhoff's Rule:

$$-L \frac{dI}{dt} - \frac{Q}{C} = 0 \rightarrow L \frac{d^2 Q}{dt^2} + \frac{Q}{C} = 0$$

Compare with: $F = ma = -kx$


$$m \frac{d^2 x}{dt^2} + kx = 0 \quad \text{solution: } x(t) = A \cos(\omega t + \phi)$$


$$L \frac{d^2 Q}{dt^2} + \frac{Q}{C} = 0 \quad \text{solution: } Q(t) = Q_{\max} \cos(\omega t + \phi), \quad \omega = \frac{1}{\sqrt{LC}}$$

$$\rightarrow I = -\omega Q_{\max} \sin(\omega t + \phi)$$

$$U = U_C + U_L = \frac{Q^2}{2C} + \frac{L}{2} I^2 = \frac{1}{2C} Q_{\max}^2 \cos^2(\omega t + \phi) + \frac{L}{2} \omega^2 Q_{\max}^2 \sin^2(\omega t + \phi)$$

$$= \frac{Q_{\max}^2}{2C}$$

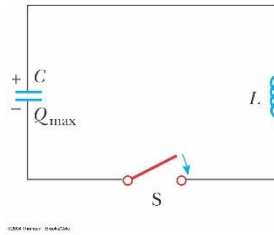


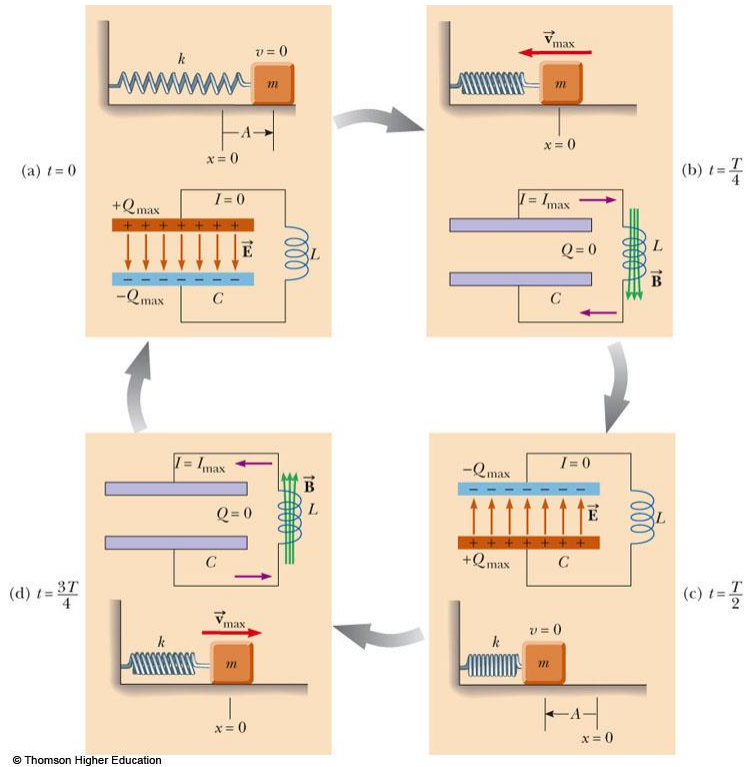

Apply the Kirchhoff's loop rule:

$$-L \frac{dI}{dt} - \frac{Q}{C} = 0$$
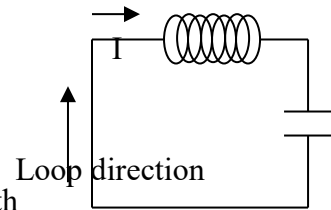
$$\rightarrow L \frac{d^2Q}{dt^2} + \frac{Q}{C} = 0 \quad (\text{2nd Differential Equation, compare with}$$



harmonic oscillation: $F = ma = m \frac{d^2x}{dt^2} = -kx$ with the answer of $x = A \cos(\omega t + \delta)$,

$$\text{where } \omega = \sqrt{\frac{k}{m}}$$

Remember the pattern of this differential equation:


$L \frac{d^2Q}{dt^2} + \frac{Q}{C} = 0$ \rightarrow the solutions are periodical functions and the useable functions are $\sin(x)$ ($\cos(x)$), $\exp(ix)$ ($\exp(x)$), ...

Guess that the answer is $Q = A \cos(Bt + C)$. (Here A and C can be determined by initial conditions.)

$$\rightarrow -LB^2 A \cos(Bt + C) + \frac{1}{C} A \cos(Bt + C) = 0 \rightarrow B = \frac{1}{\sqrt{LC}} \equiv \omega$$

$$\rightarrow Q = A \cos(\omega t - \delta) \quad \& \quad I = \frac{dQ}{dt} = -\omega A \sin(\omega t - \delta) = -I_{peak} \sin(\omega t)$$

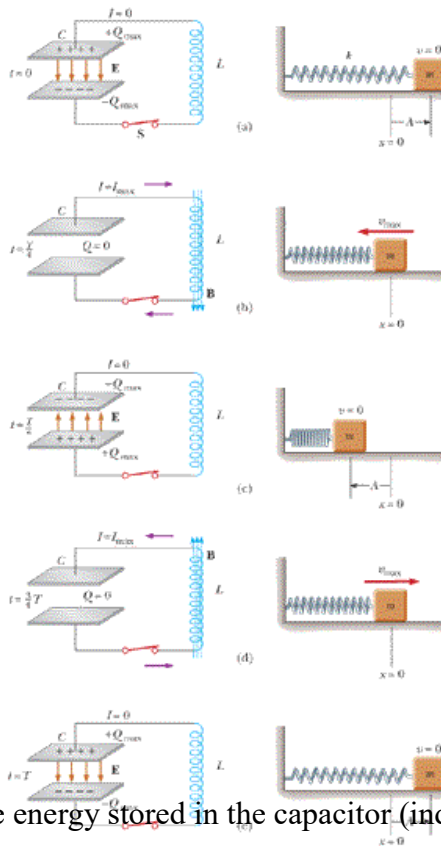Serway/Jewett; Principles of Physics, 3/e
Figure 24.9



Capacitor --> Electric Field
--> Potential Energy

Inductor --> Moving of Charges
--> Kinetic Energy

The average energy stored in the capacitor (inductor) is $\frac{Q^2}{2C}$ ($\frac{1}{2}LI^2$).

The instantaneous energy transferring in the circuit is:


$$\frac{Q^2}{2C} + \frac{1}{2}LI^2 = \frac{A^2 \cos^2(\omega t - \delta)}{2C} + \frac{1}{2}L\omega^2 A^2 \sin^2(\omega t - \delta) = \frac{A^2}{2C} = \frac{Q_{peak}^2}{2C} = \frac{1}{2}LI_{peak}^2$$

What are physical pictures of Q_{peak} and I_{peak} ?

Example: A 2- μ F capacitor is charged to 20 V and the capacitor is then connected across a 6- μ H inductor. (a) What is the frequency of oscillation? (b) What is the peak value of the current?

(a) $\omega = \frac{1}{\sqrt{LC}}$, (b) $\frac{CV^2}{2} = \frac{Q_{peak}^2}{2C} = \frac{LI_{peak}^2}{2}$

Simple AM Radio receiver:

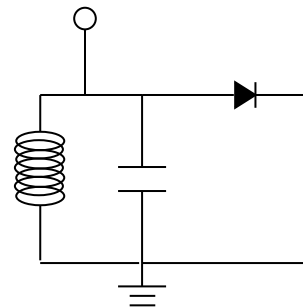

31.6 The RLC Circuit

Kirchhoff's Rule:

$$-IR - L \frac{dI}{dt} - \frac{Q}{C} = 0$$

Power Consideration:

$$P = LI \frac{dI}{dt} + \frac{Q}{C} I = -I^2 R$$

$$\rightarrow L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

Compare with damped oscillation:

$$m \frac{d^2 x}{dt^2} + b \frac{dx}{dt} + kx = 0 \rightarrow x(t) = Ae^{nt}, \quad mn^2 + bn + k = 0 \rightarrow n = \frac{-b \pm \sqrt{b^2 - 4mk}}{2m}$$

$$b^2 < 4mk \rightarrow x(t) = Ae^{-\frac{b}{2m}t} \cos\left(\frac{\sqrt{4mk - b^2}}{2m}t\right)$$


$$Q(t) = Q_{\max} e^{-\frac{R}{2L}t} \cos\left(\frac{\sqrt{4L/C - R^2}}{2L}t\right)$$

TABLE 32.1

Analogies Between Electrical and Mechanical Systems

| Electric Circuit | | One-Dimensional Mechanical System |
|--|--|---|
| Charge | $Q \leftrightarrow x$ | Position |
| Current | $I \leftrightarrow v_x$ | Velocity |
| Potential difference | $\Delta V \leftrightarrow F_x$ | Force |
| Resistance | $R \leftrightarrow b$ | Viscous damping coefficient |
| Capacitance | $C \leftrightarrow 1/k$ | (k = spring constant) |
| Inductance | $L \leftrightarrow m$ | Mass |
| Current = time derivative of charge | $I = \frac{dQ}{dt} \leftrightarrow v_x = \frac{dx}{dt}$ | Velocity = time derivative of position |
| Rate of change of current = second time derivative of charge | $\frac{dI}{dt} = \frac{d^2 Q}{dt^2} \leftrightarrow a_x = \frac{dv_x}{dt} = \frac{d^2 x}{dt^2}$ | Acceleration = second time derivative of position |
| Energy in inductor | $U_L = \frac{1}{2}LI^2 \leftrightarrow K = \frac{1}{2}mv^2$ | Kinetic energy of moving object |
| Energy in capacitor | $U_C = \frac{1}{2}\frac{Q^2}{C} \leftrightarrow U = \frac{1}{2}kx^2$ | Potential energy stored in a spring |
| Rate of energy loss due to resistance | $I^2 R \leftrightarrow bv^2$ | Rate of energy loss due to friction |
| RLC circuit | $L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0 \leftrightarrow m \frac{d^2 x}{dt^2} + b \frac{dx}{dt} + kx = 0$ | Damped object on a spring |

RLC Circuit (Damped Oscillation)

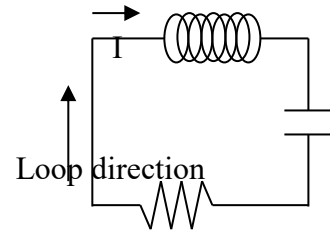

$$\text{Diff Eq: } -L \frac{dI}{dt} - \frac{Q}{C} - IR = 0$$


$$\rightarrow L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0 \quad (\text{Damped Oscillations: } F = ma = -kx - bv)$$

$$\text{The natural frequency (no resistor) is: } \omega_0 = \frac{1}{\sqrt{LC}} \quad (L \frac{d^2Q}{dt^2} + \frac{Q}{C} = 0).$$

We guess a solution of $Q = Ae^{Bt}$ for solving the differential equation


$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0.$$
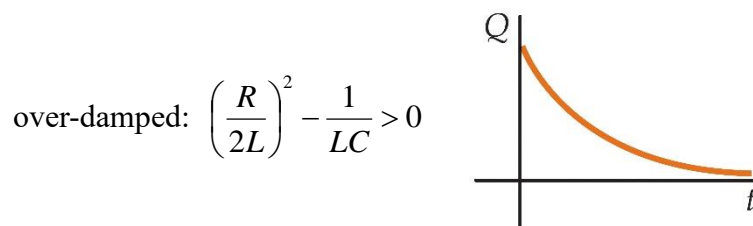
$$\left(LB^2 + RB + \frac{1}{C} \right) Ae^{Bt} = 0 \quad \rightarrow \quad B = \frac{-R \pm \sqrt{R^2 - 4\frac{L}{C}}}{2L} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$



under-damped: $\left(\frac{R}{2L}\right)^2 - \frac{1}{LC} < 0$

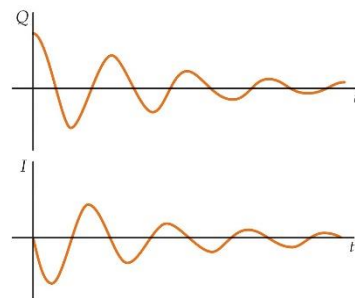under-damped solution: $Q = Ae^{-\frac{R}{2L}t} e^{\pm i\sqrt{\omega_0^2 - \left(\frac{R}{2L}\right)^2}t}$



The energy distributed in the circuit elements is:

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0 \quad \rightarrow \quad LI \frac{dI}{dt} + RI^2 + \frac{Q}{C} \frac{dQ}{dt} = 0$$

$$\rightarrow \frac{d}{dt} \left(\frac{1}{2} LI^2 + \frac{Q^2}{2C} \right) + I^2 R = 0$$